

Sheet 2
Electronic Circuits & Measurements

Feedback

8.1

- Q1 A -ve FB amplifier has a closed loop gain $A_f = 100$ and an open-loop gain $A = 10^5$. What is the feedback factor β ? If a manufacturing error results in a reduction of A to 10^3 , what closed loop gain results? What is the % change

8.2 in A_f corresponding to this factor of 100 reduction in A ?

8.5

- Q2 For the -ve FB structure, find the loop gain AB for which the sensitivity of closed loop gain to open loop gain $[(dA_f/A_f)/(dA/A)]$ is -20dB. For what value of AB does the sensitivity become $\frac{1}{2}$?

- Q3 A particular amplifier has a non-linear transfer char that can be approximated as follows

a) for $|V_I| \leq 10 \text{ mV}$ $V_O/V_I = 10^3$

b) for $10 \text{ mV} \leq |V_I| \leq 50 \text{ mV}$ $V_O/V_I = 10^2$


c) for $|V_I| \geq 50 \text{ mV}$ V_O saturates

If the amplifier is connected in a -ve FB loop, find the FB factor β that reduces the factor of 10 change in gain to only a 1% change. What is the transfer char of the amplifier with FB?


- Q4 A series-shunt FB amplifier. Using $V_s = 100 \text{ mV}$, $V_{f, \text{max}} = 90 \text{ mV}$ and $V_o = 10 \text{ V}$. What are the corresponding values of A and β ?

8-9

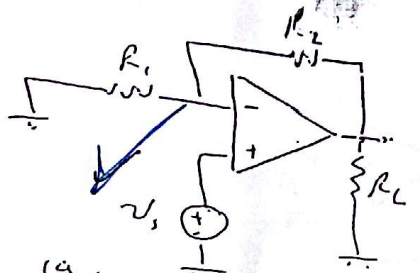
(15) For each of the following op-amp circuits, identify the feedback topology. Indicate the output variable being sampled and the feedback signal. Find expression for β and hence find A_f .




(a) series-shunt

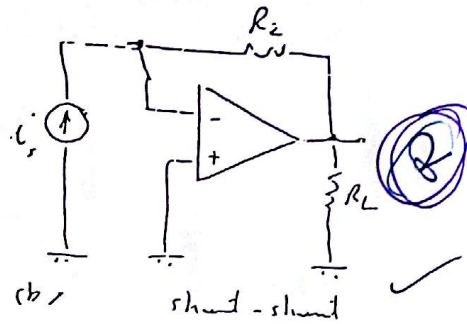

(b) shunt-shunt

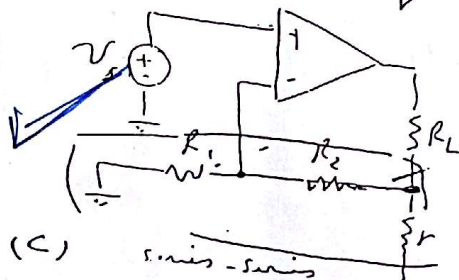

(c) series-series

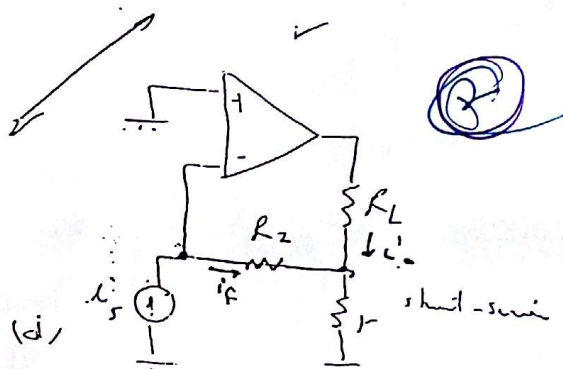

(d) shunt-series


8-20

27

(6) A series-shunt FB amplifier employs a basic amplifier with input and output resistances each of $1\text{ k}\Omega$ and gain $A = 2000\text{ V/V}$. The FB factor $\beta = 0.1\text{ V/V}$. Find the gain, A_f , and i_{ip} and o_{ip} resistances R_{if} , R_{of} .

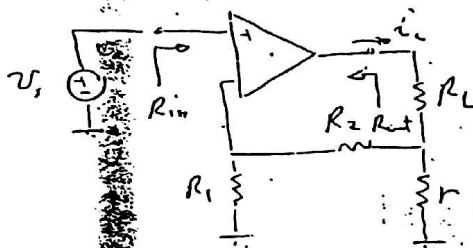(7) A series-series FB amplifier employs a transconductance amplifier having $G_m = 100\text{ mA/V}$; i_{ip} resistance of $10\text{ k}\Omega$, and o_{ip} resistance of $100\text{ k}\Omega$. The FB network has $\beta = 0.1\text{ V/mA}$, an i_{ip} resistance (with port 2 open-circuited) of $100\text{ k}\Omega$, and an o_{ip} resistance (with port 2 open-circuited) of $10\text{ k}\Omega$. The amplifier operates with a signal source having $R_{sig} = 10\text{ k}\Omega$, and with $R_L = 10\text{ k}\Omega$. Find A_f , R_{in} , R_{out} .

Q. For the series-series FB amplifier shown, the op-amp is characterized by an open-loop voltage gain μ , $R_{id} = 10 \text{ k}\Omega$, $r_o = 100 \Omega$, $R_L = 1 \text{ k}\Omega$. The FB network has $R_1, R_2 = 10 \text{ k}\Omega$, and $r = 100 \Omega$. Find $A_f = i_o / v_s$, R_{in} , R_{out} for: a) $\mu = 10^5 \text{ V/V}$, $R_1 = 10 \text{ k}\Omega$
b) $\mu = 10^4 \text{ V/V}$, $R_1 = 10 \text{ k}\Omega$




- Q. For the amplifier network shown
- Identify the FB connection type
 - Draw the equivalent circuit of the amplifier considering the loading effect of the FB circuit
 - Find expressions, then calculate the numerical values for A , β , A_f , R_{if} , and R_{of} .

given: $R_L = R_D = 10 \text{ k}\Omega$

$g_m = 4 \text{ mA/V}$, $r_o = 100 \text{ k}\Omega$

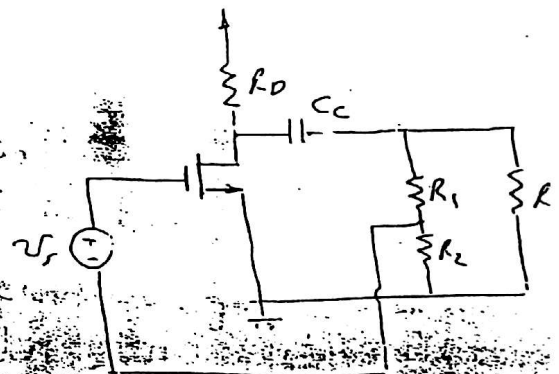$R_1 = 80 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$



Chapter (3)

Feed back.

*What is feedback

المقصود بـ feedback هو أخذ جزء من الخرج وبيتم ارجاعه مرة اخرى الى الدخل

-ve feedback

اذا تم ارجاعه الى الـ IP موجب

+ve feedback

الب

-ve F.B
used in
amplifier


&

+ve F.B
used in
oscillators

-ve F.B → feedback signal is out of phase of i/p
phase shift = 180°

+ve F.B → " " " " in phase " "
phase shift = 0°

*The General feedback structure

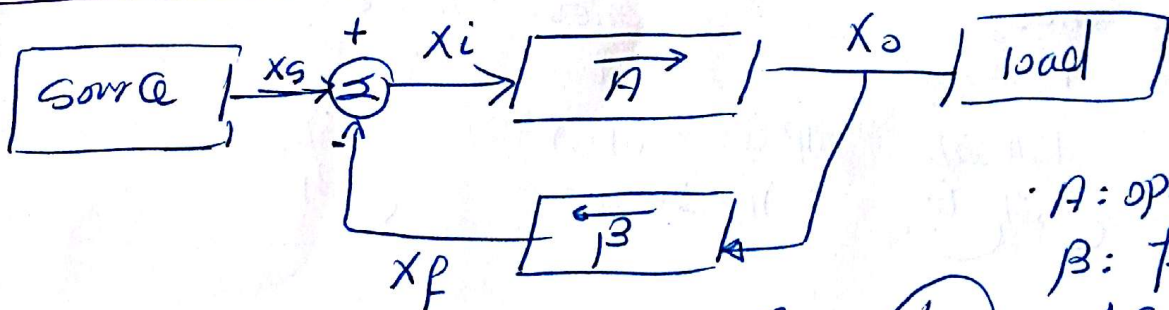

A: open loop Gain
β: feedback parameter
AB: Loop Gain

$$A_f = \frac{A}{1 + AB} \quad AB \gg 1 \quad \approx \frac{A}{AB} \approx \left(\frac{1}{\beta} \right)$$

* feedback types There are 4 types of feedback

↳ series-shunt

↳ series-series

↳ shunt-shunt

↳ shunt-series

↓

↓


input

output

Series - Shunt Feed back

دور معناه
series في ال
i/p

دور معناه
shunt في ال
o/p

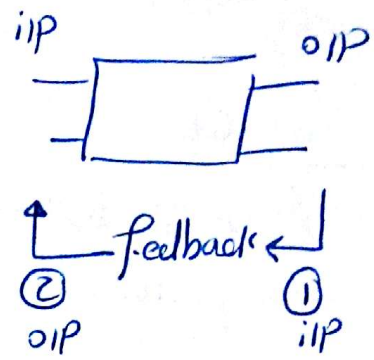

Note

Current feedback = series o/p
لذلك تنقسم

عند ①
عازل اعمل feedback لتيار الخرج
: توافك هافذ I_o

Voltage feedback = parallel i/p
لذلك تنقسم

عازل اعمل feedback لجهد الخرج
: توافك هافذ V_o

Called shunt
Called series

لختيار في الدخل : ادخل توافك في نقطة الدخل
لجهد في الدخل : ادخل توافك مع الدخل

Series - Series
↑ ↑

بدخل على أني
جهد في الدخل
لافذ التيار
بتفاع الخرج

series - shunt
↑ ↑

ادخل على أني
جهد في ال o/p
لافذ جهد
الخرج

خ المعاضه
analysis
ايجاد

model , R_{i1} , R_{o1} , A_F , β
+ R_{i1} , R_{22}

1] -ve F-B, $A = 10^5$ "open loop gain" $A_f = 100$ Find feedback factor β ??

manu factoring error in $A \rightarrow A_{new} = 10^3$

what is the closed loop gain

what is the % change in A_f

$$A_f = \frac{A}{1+A\beta} \rightarrow A\beta = \frac{A}{A_f} - 1 = \frac{10^5}{100} - 1 = 999$$

$$\beta = \frac{999}{10^5} = 9.99 \times 10^{-3} \#$$

$$\bullet \text{ at } A = 10^3 \rightarrow A_f = \frac{A}{1+A\beta} = \frac{10^3}{1 + 10^3 \times (9.99 \times 10^{-3})}$$

$$A_f = 90.99$$

$$\frac{dA_f}{A_f} = \frac{A_{f_{new}} - A_{f_{old}}}{A_{f_{old}}} = \frac{90.99 - 100}{100} \times 100 = -9\% \#$$

2] -ve F-B, Find Loop Gain $A\beta$, sensitivity of $\frac{\text{closed loop gain}}{\text{open loop gain}}$ for what value of $A\beta$ does the sensitivity become $\frac{1}{2}$ = -20 dB

$$\bullet \frac{dA_f}{A_f} / \frac{dA}{A} = \frac{1}{1+A\beta} = \text{sensitivity} = -20 \text{ dB}$$

$$= 1+A\beta = 20 \text{ dB}$$

$$20 \log(1+A\beta) \Big|_{\text{ratio}} = 20 \text{ dB}$$

$$1+A\beta = 10$$

$$A\beta = 9 \#$$

$$\bullet \frac{1}{1+A\beta} = \frac{1}{2}$$

$$1+A\beta = 2$$

$$A\beta = 1 \#$$

amplifier has particular non linear CLC
can be approximated as follows

- for small signal $\rightarrow |V_i| < 10\text{mV} \rightarrow \frac{V_o}{V_i} = 10^3$
- for intermediate input signal $\rightarrow 10\text{mV} \leq |V_i| \leq 50\text{mV} \rightarrow \frac{V_o}{V_i} = 10^2$
- for large signal $\rightarrow |V_i| \geq 50\text{mV}$

• The amplifier connected in $-ve$ F.B \rightarrow Final β The o/p saturated

Feedback factor ??
that reduce the factor of gain to only 10% change (at $V_i = 10\text{mV}$) occurring ab

• what is the CLC of amplifier with F.B ??

reduce = 10%
remain = 90%

$$A_{f2} = 0.9 A_{f1}$$

$$\frac{100}{1+100\beta} = 0.9 \frac{10^3}{1+10^3\beta} \rightarrow \beta = 0.08$$

$$A_f = \frac{A}{1+A\beta}$$

$$A_{f1} = \frac{10^3}{1+10^3(0.08)} = 12.84 \rightarrow |V_i| \leq 10\text{mV}$$

$$A_{f2} = \frac{10^2}{1+10^2(0.08)} = 10.1 \rightarrow 10\text{mV} \leq |V_i| \leq 50\text{mV}$$

Then o/p saturated $\rightarrow |V_i| \geq 50\text{mV}$

Now

$$\frac{V_i}{A=10^3} \rightarrow \frac{V_i}{A=10^2}$$

Feedback

$$\frac{V_i}{A_f=12.4} \rightarrow \frac{V_i}{A_f=10}$$

معدل التغير في A_f أقل من معدل تغير A

Series-shunt $\sqrt{\beta}$
 amplifier \rightarrow i/p & o/p resistors = 1K
 gain = $A = 2000$ V/V

Feedback parameter $\beta = 0.1$ V/V


Find A_{f2} in p, out p R_{if} of R_{of}

$$A_f = \frac{A}{1+A\beta} = \frac{2000}{1+2000 \times 0.1} \quad \#$$

$$R_{if} = R_i(1+A\beta) = 1K [1+2000 \times 0.1]$$

$$R_{of} = \frac{R_o}{1+A\beta} = \frac{1K}{(1+2000 \times 0.1)} \quad \#$$

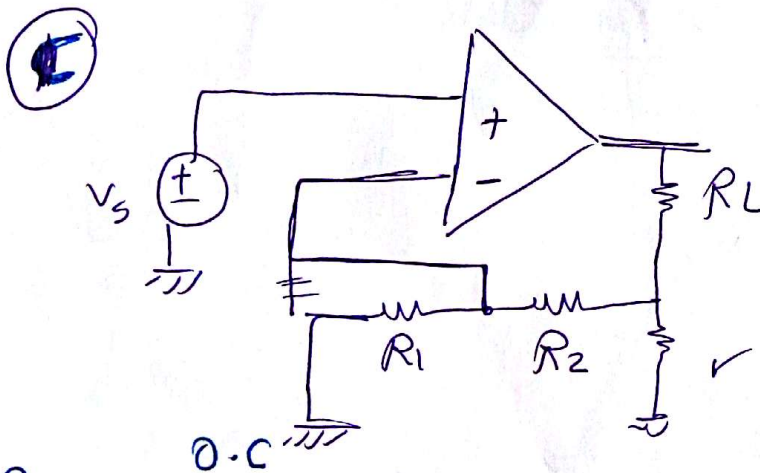5 For each of the following op-amp
 \rightarrow identify feedback topology
 \rightarrow Find expression for β and then A_f



$R_L \Rightarrow$ open circuit

$I_f = 0$ \therefore Current Feedback

series & o/p

ویرجیٹ کی ال پ پ ا فیڈبک - : تو

Series-series


لتیید النوع
 \rightarrow put $R_L = o.c$
 if the signal returned
 to the amplifier i/p
 by feedback = 0

\therefore Current feedback

\rightarrow put $R_L = s.c$

 ----- = 0

\therefore voltage feedback

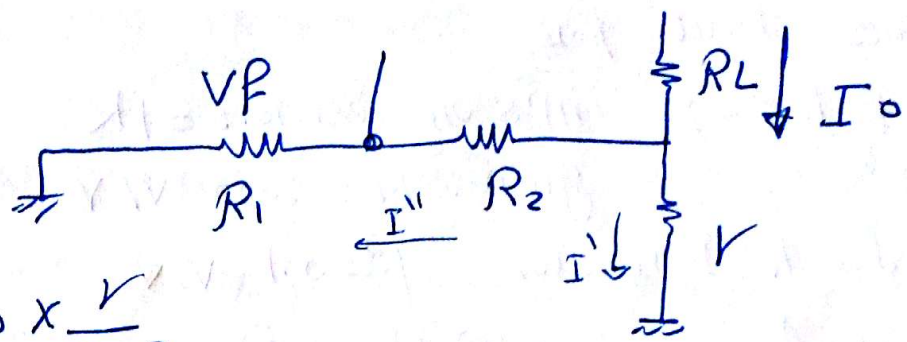


$$I'' = I_0 \times \frac{V}{R_1 + R_2}$$

$$V_F = I'' R_1 = \frac{I_0 V R_1}{R_1 + R_2}$$

$$\beta = \frac{V_F}{I_0} = \frac{V R_1}{R_1 + R_2} \neq$$

$$A_f \approx \frac{1}{\beta} = \neq \frac{R_1 + R_2}{V R_1} = \left[\frac{1}{V} + \frac{R_2}{V R_1} \right] \neq$$

(a)

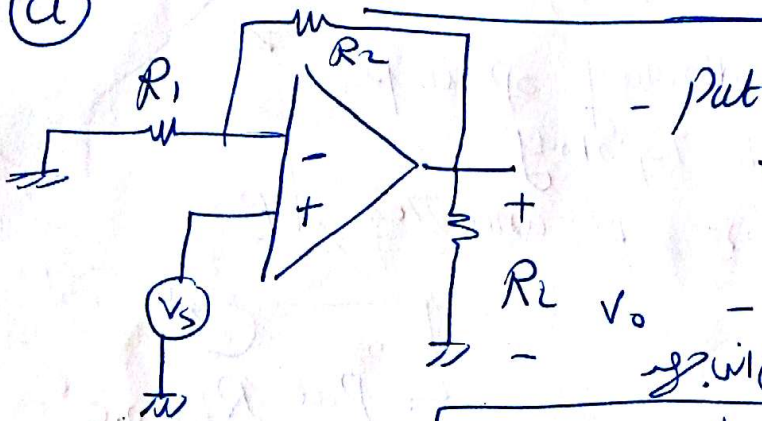


- put $R_L \Rightarrow S.C$

$$V_F = 0$$

\rightarrow voltage feedback
shunt \rightarrow o/p

- voltage divider
series in i/p

series-shunt

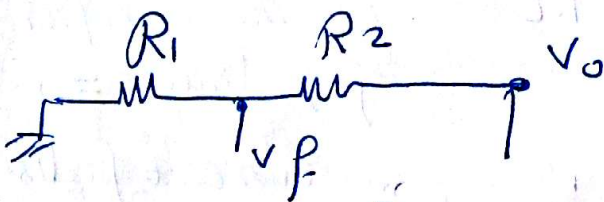

$$V_F = V_0 \times \frac{R_1}{R_1 + R_2}$$

$$\frac{V_F}{V_0} = \beta = \frac{R_1}{R_1 + R_2} \neq$$

$$A \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} \neq$$




sec
Feed back

Series-shunt Feedback

دور مدار جری
فصل ال دخل
دور مدار
خارج

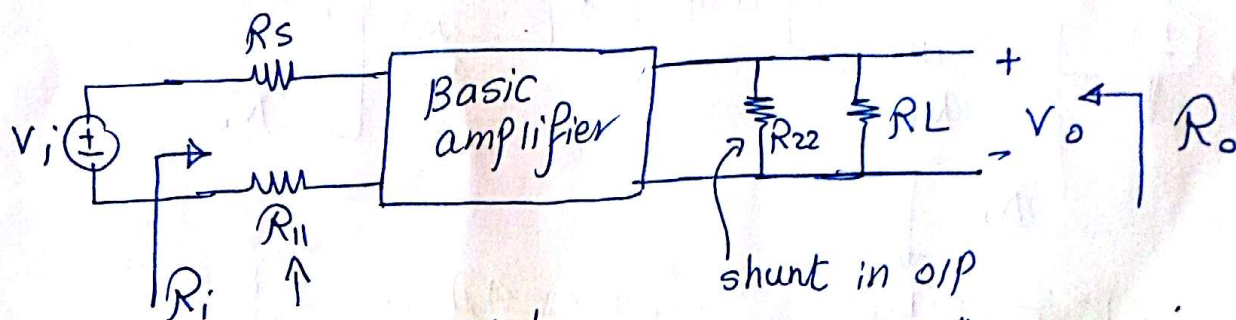o/p
y.p
 $A \rightarrow$ voltage gain $A_v = \frac{V_o}{V_i}$





series in input
القائمة تتصل بتوازي

الذين دخل تتصل بوجوده

Feed back circuit

* To find R_{11}

* To find R_{22}

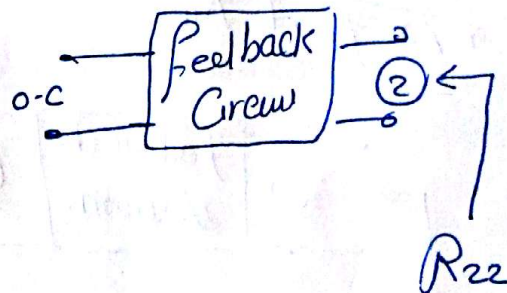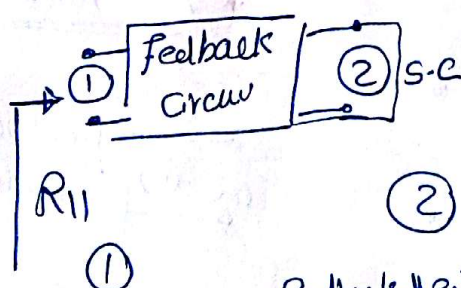

دور ال Feedback
هو هو خرج ال amplifier
Feedback ال amplifier

* To find β


$$\beta = \frac{V_f}{V_o}$$

o/p amplifier
i/p feedback
shunt



Series. Series Feedback

↓ ↓
 ده معناه ده معناه
 في الدخل في اخرج

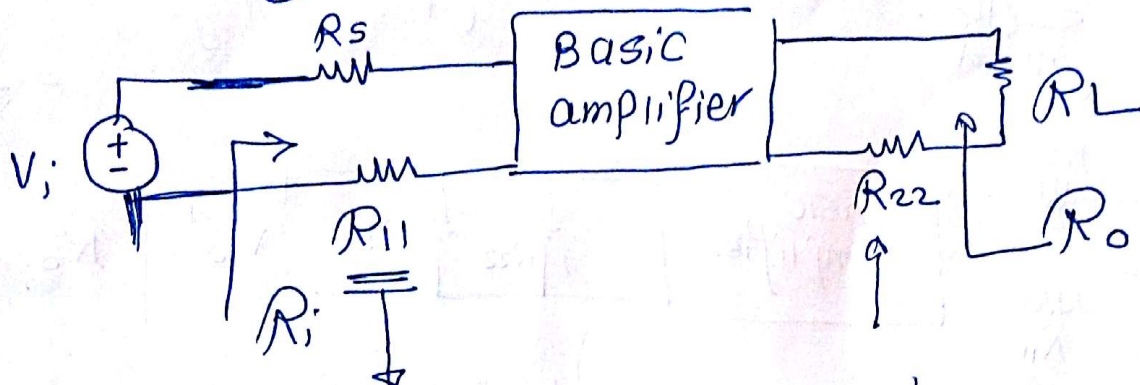

في اوقات صان
 i/p series

في اوقات صان
 o/p series

*


i/p




o/p

$$A \equiv \frac{I_o}{V_i} = \text{TransConductance.}$$


* To find R_{ii}

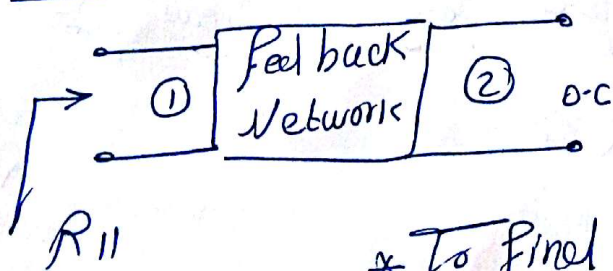

* To find R_{22}

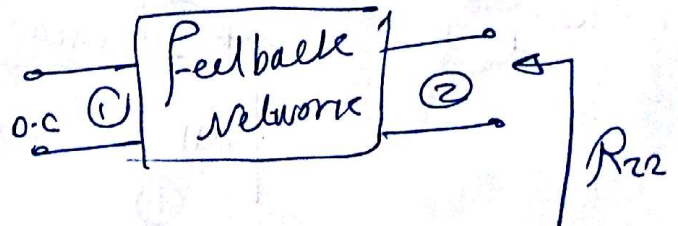

* To find β

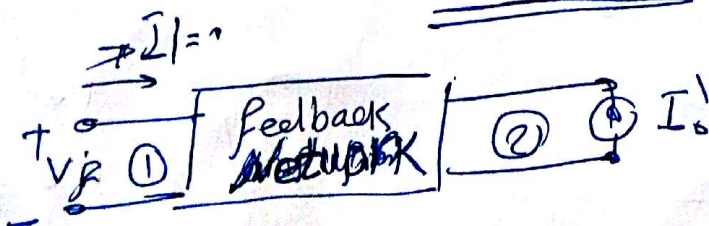

$$\beta = \frac{V_p}{I_o}$$

$$A_f = \frac{A}{1+A\beta} = \frac{100 \frac{mA}{V}}{1 + \frac{100 mA}{V} \times 0.1 \frac{V}{mA}} =$$

$$R_{in} = R_{if} - R_s \quad R_{out} = R_{of} - R_L$$

$$R_{if} = R_i (1+A\beta) \quad R_{of} = R_o (1+A\beta)$$

$$R_i = R_s + R_{if} + R_{ii} \quad R_o = R_L + R_{of} + R_{oz}$$

8 Series-series μ V \cdot I β
Voltage Gain μ
 $R_{id} = 10K \quad R_o = 10$

$$F_{med} A_f = \frac{i_o}{V_s}$$


$\frac{R_{in}}{R_{out}}$

a) $\mu = 10^5 V/V$

$R_1 = 100 \Omega$

b) $\mu = 10^4 V/V$

$R_1 = \infty$

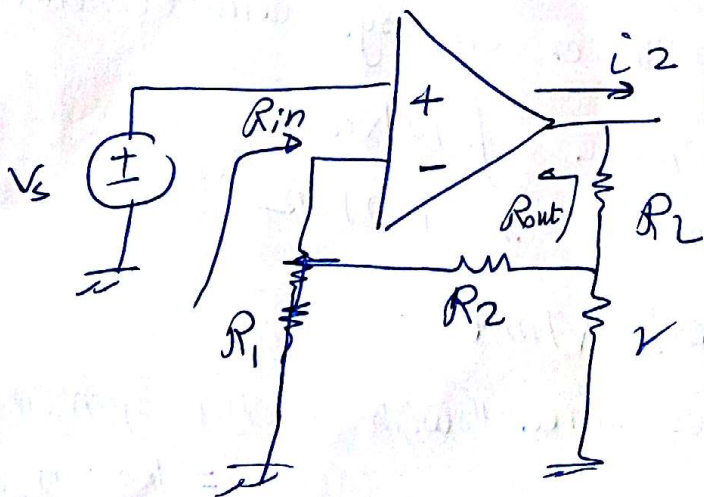


- 9) a) identify F.B Connection type
 b) Draw equivalent Circuits of amplifier + feedback
 c) expression and Calculate
 $A, \beta, A_f, R_{if}, R_f$

$$R_L = R_S = 10 \text{ k}\Omega$$


$$g_m = 4 \text{ mA/V} \quad V_0 = 100 \text{ V}$$
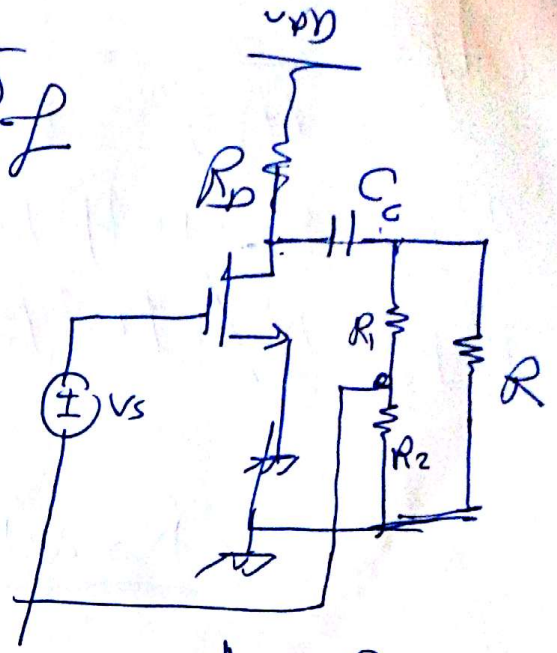
$$R_1 = 20 \text{ k}\Omega \quad R_2 = 20 \text{ k}\Omega$$



b) ac analysis

a) series-shunt

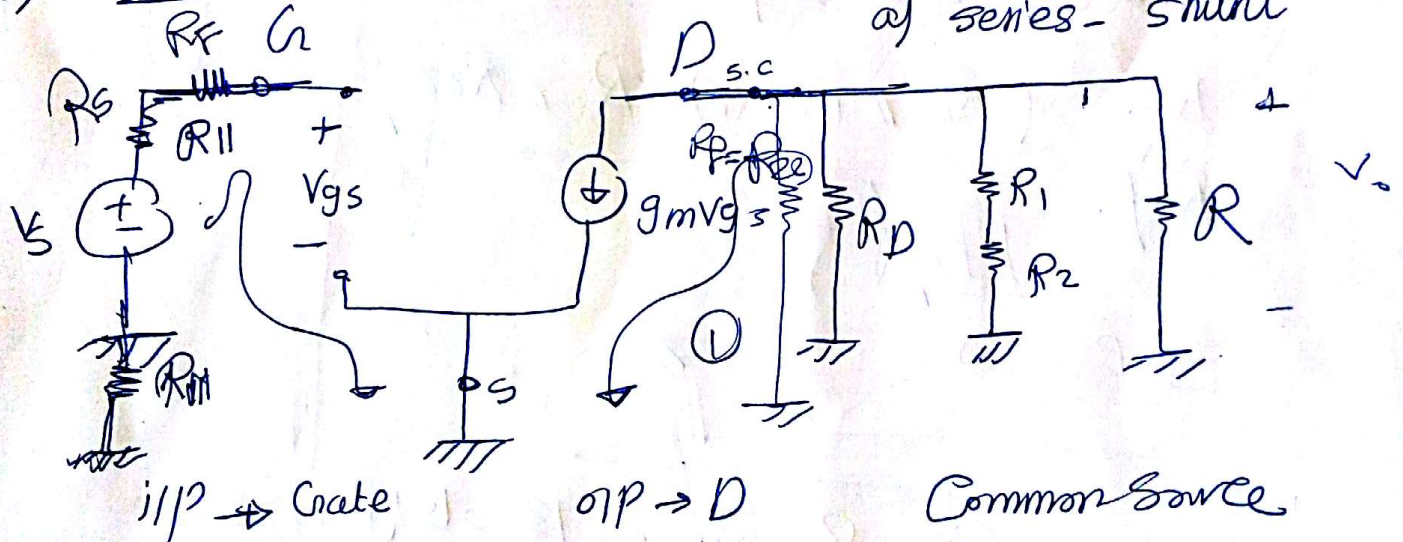

$$A_v = \text{voltage gain} = -g_m R_{\text{Drain}}$$

at K.V.L ①

$$V_0 = -(g_m V_{gs}) \times [R_D \parallel (R_1 + R_2) \parallel R_{if} R_{22}] \quad ①$$

at K.V.L ②

$$V_{in} - V_{gs} = 0 \rightarrow V_{in} = V_{gs} \quad ②$$

$$A_v = \frac{V_0}{V_{in}} = \frac{-g_m V_{gs} [R_D \parallel (R_1 + R_2) \parallel R_{if} R_{22}]}{V_{gs}} = -g_m [\dots]$$

$$A = -g_m [R_D \parallel (R_1 + R_2) \parallel R \parallel R_{22}]$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-g_m [R_D \parallel (R_1 + R_2) \parallel R]}{1 + (-g_m [R_D \parallel (R_1 + R_2) \parallel R]) \beta}$$

$$R_{if} = R_i (1 + A\beta) \rightarrow R_{in} = R_{if} - R_s \neq$$

$$R_{of} = R_o / (1 + A\beta) \rightarrow R_{out} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}} \neq$$

\Downarrow
 R_o & R_i is


$$R_i = \infty \rightarrow R_{if} = \infty \rightarrow R_{in} = \infty$$

$$R_o = (R_D \parallel (R_1 + R_2) \parallel R \parallel R_{22})$$

$$R_{of} = \frac{R_o}{1 + A\beta}$$


$$R_{if} = \infty \neq$$

R_{22} & R_{11} & β is is is

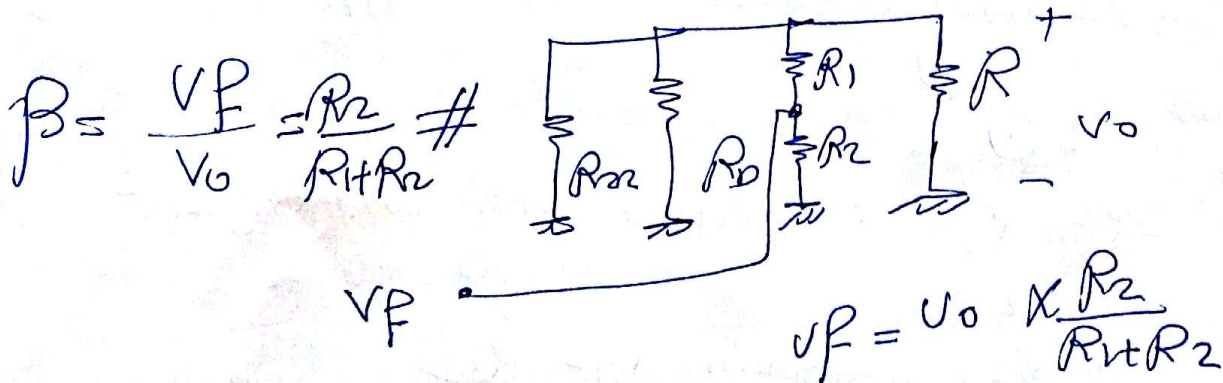


R_{22}

الفروع

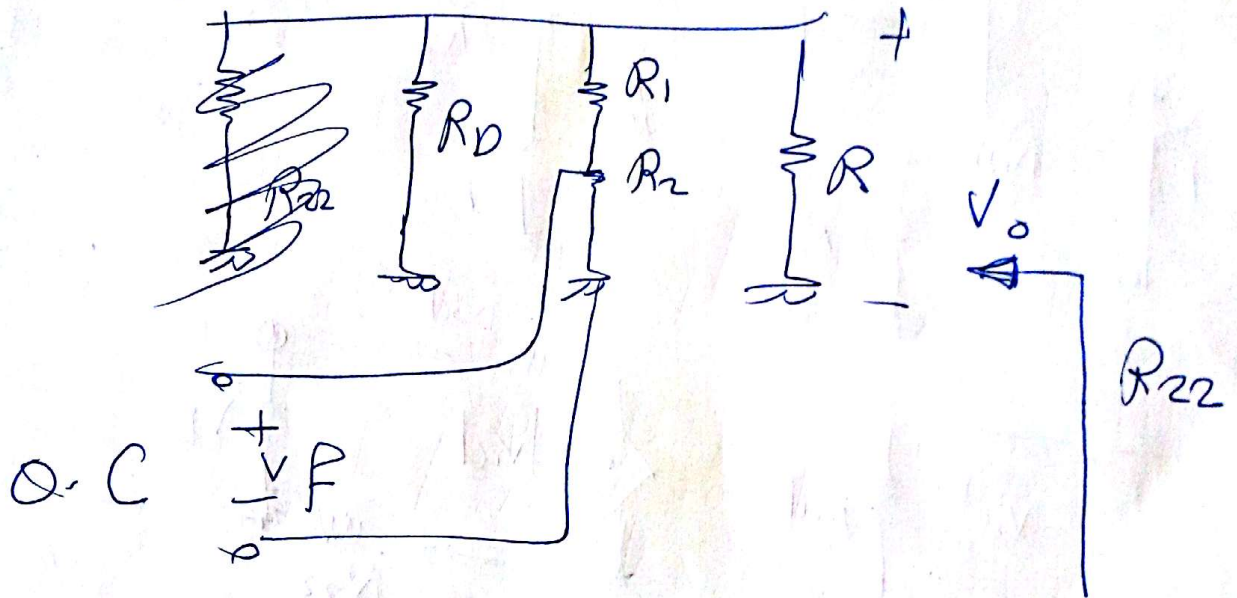
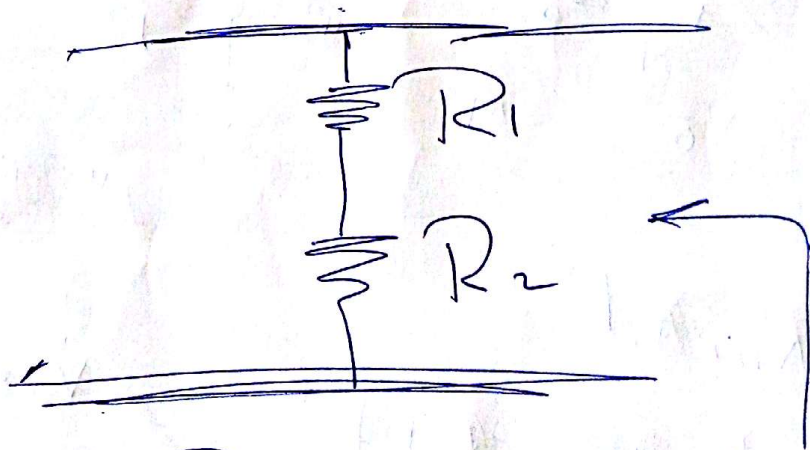
$$R_{22} = R \parallel R_1 \parallel R_2 \parallel R_0$$



$$R_{22} = \frac{R_1 + R_2}{2}$$